

Audio Classroom

Designing Your Own Amplifier, Part 5: Feedback Amplifiers

BY NORMAN H. CROWHURST

This article appeared originally in Audiocraft, October 1956. ©1956 by Audio.com, Inc.

There are so many matters to consider in the design of a feedback amplifier that discussion of them will get rather confusing unless we use a practical amplifier for illustration. In this article let us work with the schematic diagram in Fig. 1, which shows the outline of a circuit with the components identified by numbers, and complete the design of this feedback amplifier step by step, filling in the values as we determine them. In this way we shall be sure to cover the practical problems that have to be solved.

A good feedback amplifier cannot be obtained by designing a reasonably good amplifier and then adding feedback for good measure. This approach, believe it or not, can sometimes produce an amplifier with greater distortion than one that does not employ feedback. The first thing to do is to go through the amplifier, starting at the output, and calculate the operating conditions for the tubes and the maximum levels they will handle, incorporating or allowing for feedback as we go.

OUTPUT STAGE

Let's assume that we are designing a good 20W amplifier. For self-biased 6L6s in the output stage, the tube data manual shows the following tabulation of operating conditions for 24W output, with an optimum load of 9,000Ω.

6L6s IN CLASS AB ₁ (Values for two tubes)		
	Zero Signal	Maximum Signal
Plate voltage	360V	360V
Plate current	88mA	100mA
Screen voltage	270V	270V
Cathode resistor	250Ω	250Ω
Load	9k	9k

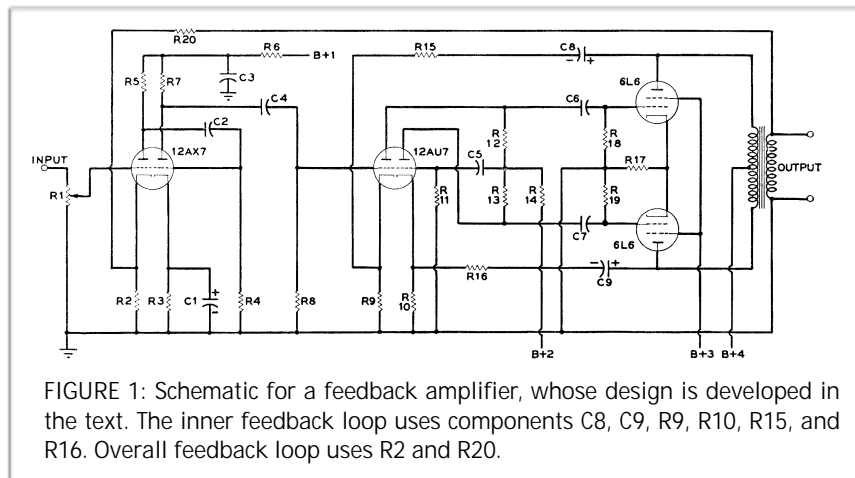


FIGURE 1: Schematic for a feedback amplifier, whose design is developed in the text. The inner feedback loop uses components C8, C9, R9, R10, R15, and R16. Overall feedback loop uses R2 and R20.

Power output — 24W
Harmonic dist. — 4%

We will assume that we shall use such an output circuit. That sets the cathode bias resistor, R17, at 250Ω.

This 24W in the plate circuit will be mean or average maximum watts, so the peak value will be twice this, or 48W. The formula $W = V^2/R$ can be altered to the form $V = \sqrt{WR}$, to determine the peak maximum-signal voltage across the primary winding of the output transformer. This is $\sqrt{48 \times 9,000}$, or 650. Then there will be a peak voltage of 325V on each half of the primary. We shall need this figure presently to calculate the inner feedback loop values of R15 and R16.

Next we move back to the grid circuit of the output stage. The total cathode current of the two 6L6s at maximum output is just under 120mA. This current, in the 250Ω bias resistor, will produce a bias of 29V at maximum signal; which means the peak drive to each grid for maximum output also needs to be 29V.

DRIVE STAGE; INNER LOOP

The 12AU7 tube, shown in the drive stage, is similar to the 6SN7 except that it happens to be of the miniature type. In the article on the design of phase inverters (*Glass Audio* 2/00, p. 48) it was found that a floating paraphase circuit could quite successfully provide a drive of about 29V to each output-tube grid with a plate supply of 250V. We can obtain a

good safety margin here by utilizing the plate supply for the 6L6s for the B+ to the 12AU7 tube, which is 360V. This will prove convenient, because the feedback places extra demands on the paraphase action, as we shall see in a moment.

Using a plate-load resistor of 100k, with a cathode resistor of 2.2k and a plate supply of 250V at the junction of the three resistors R12, R13, and R14, will give a gain of approximately 13. These values will produce 3.7V bias with 1.7mA plate current. The plate current of two tubes will be 3.4mA, and the drop in the common resistor, R14, will be 110V, from 360 to 250. This means that R14 should be about 33k.

Now we must digress a moment to consider the voltages involved in the inner feedback loop. The purpose of this loop is to reduce the plate resistance of the output stage to a point at which variations in output load impedance will not cause appreciable changes in the outer-loop feedback, thereby improving stability under varying load conditions. The plate resistance of the tubes is not listed, because it varies widely over the operating distance of the load line. A good estimate, however, would be that its average value throughout a signal cycle will not vary much more than about five times the optimum load resistance. Thus, if we can reduce this effective ratio by 5:1, using the inner loop, a change of load impedance from optimum value to open circuit will only change the outer-loop

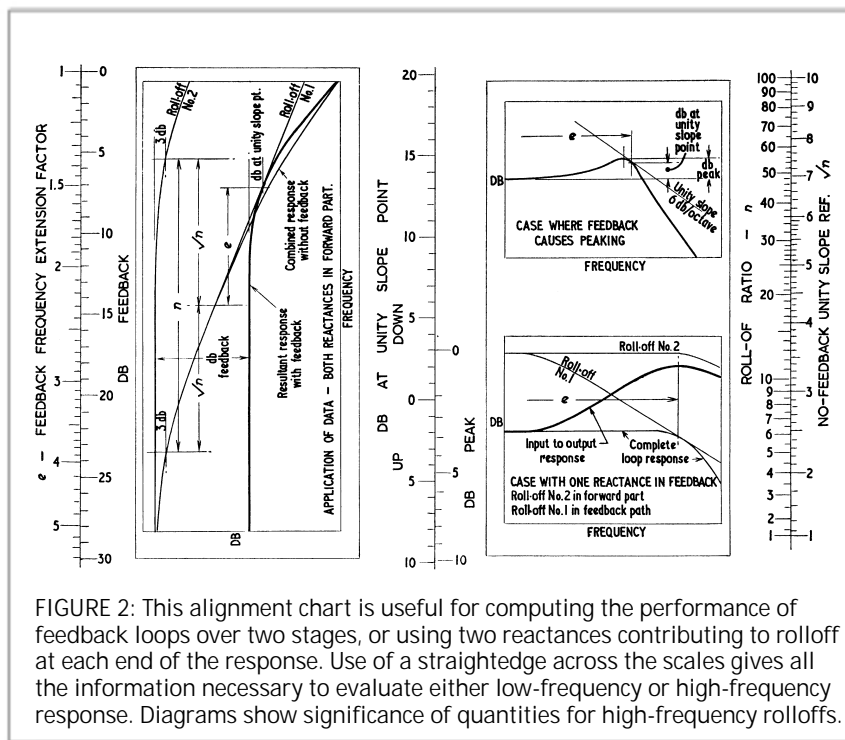


FIGURE 2: This alignment chart is useful for computing the performance of feedback loops over two stages, or using two reactances contributing to rolloff at each end of the response. Use of a straightedge across the scales gives all the information necessary to evaluate either low-frequency or high-frequency response. Diagrams show significance of quantities for high-frequency rolloffs.

feedback by a 2:1 factor. This is an economic point to choose: further reduction will make unreasonable demands on the drive stage that will not produce commensurate advantage in the outer-loop stability; less reduction *will* sacrifice much in potential outer-loop stability.

Having settled that we need a 5:1 gain reduction by this inner loop, we can figure values and voltages. A gain of 13 from grid to plate of 12AU7 means that its grid-to-cathode swing has to be approximately $29/13 = 2.2V$. To reduce gain by 5:1, the grid-to-ground voltage must be $5 \times 2.2 = 11V$, while the cathode-to-ground voltage will be the difference, 8.8V. To get 8.8V across the cathode resistors, R9 and R10, from the 325V on the output-tube plates, the feedback resistors R15 and R16 must be $2.2k \times 325/8.8 = 81k$. The nearest preferred value is 82k, which will be close enough.

A voltage of 325 across a resistance of 82k works out to almost 1W peak dissipation, so 1W resistors should be used. This indicates that these feedback resistors will absorb about 1W of available output, so if the output transformer is reasonably good, there should still be 20W left at the secondary.

The left-hand half of the 12AU7 will get its 11V grid-to-ground drive from the previous stage, but the right-hand half gets it from the floating paraphase junction.

The junction of the three plate resistors coupled to the grid of the second half of the 12AU7 by C5 has to produce a

swing of 11V to match that of the first half; this must be produced by having the plate current swing of the first half greater than that of the second half by a sufficient amount to produce an 11V swing in R14.

With our assumed plate-load resistors, 100k, and a plate swing of 29V, each tube should have a swing of about 0.35mA. To get a swing of 11V across the 33k resistor R14, we need a *difference* in swing of 0.33mA. If we choose values such that the average swing is 0.35mA, and the difference in swing is 0.33mA, we will need a swing of 0.52mA on the first half tube and 0.18mA on the second half tube. This you can figure by algebra or by any method you prefer.

The first, or left-hand, half of the 12AU7 must produce 29–11V across R12, because the 11V is in phase with this output; the current swing is 0.52mA, so R12 should be $18/0.52 = 35k$. 33k at 5% would be near enough. For the right-hand half, the current swing is to be 0.18mA; the voltage swing, $29 + 11 = 40V$, so R13 must be $40/0.18 = 220k$. This will provide equal drive for both output grids. The operating conditions of the two halves of the 12AU7 will differ slightly, but any residual differences can now be taken care of by feedback, using close-tolerance values for resistors R9, R10, R15, and R16.

Thus we have now calculated the important values associated with the 12AU7 and 6L6 tubes. The grid resistors, R18 and R19, can be 330k. This will be an approxi-

mate compromise between shunting down the 12AU7 too much and providing too high a resistance in the grid circuits of the 6L6 tube. The grid resistor, R11, can be 1M Ω , to avoid shunting to any appreciable extent the 11V provided by the difference current. We shall consider R8 in the design of the 12AX7 amplifier stage.

FIRST STAGE; OVERALL FEEDBACK
Turning to the 12AX7 data, we find that, with a plate resistor of 100k, a plate-supply voltage of 180V, and the following grid resistor of 470k, each tube section gives a gain of 52 and a peak output of 32V. Since we require only a peak of 11V, this gives a margin of approximately 3:1; distortion should be well down even before feedback is applied. The cathode resistor recommended with the following grid resistor of 470k is 2,200 Ω . This data was obtained from the RCA tube manual. Similar information could be obtained from any other manual, although the figures may differ a little, or data could be based on published curves as described in earlier articles.

Two stages, each giving a gain of 52, will produce a total overall gain of about 2,700. If the output from these stages is to be 11V, the input must be about 4mV.

We would like to end up with a damping factor of about 10. Therefore we must use about 20dB overall feedback, which will reduce the gain by a ratio of 10:1 and increase the damping factor, at present approximately unity, by ten times. This means that we will need to supply a signal of 36mV peak across R2 from the secondary of the output transformer.

Assuming the output transformer is designed to match from 9,000 Ω to 16 Ω , the simplest way of calculating the voltage that should appear on its secondary is to figure out what voltage gives 20W across 16 Ω . This is 40W, since we are working in peak voltages, so the voltage will be $\sqrt{40 \times 16} = 25V$, approximately. Again working by voltage ratio, if we have 36mV across 2.2k Ω , R20 will need to be $25,000/36 \times 2.2k = 1.5M\Omega$.

This has given us all the resistance values in the circuit except R6, which we will consider later.

We now know that the amplifier will be driven to full output by an input of 40mV peak, which is about 28mV RMS. This is quite a convenient input, because it will produce full output on some low-level inputs. We might want to use a pre-amp, however, in which case 28mV would be too small an input: most pre-amps have a normal output in the region of 1V. To take care of this, we can insert a

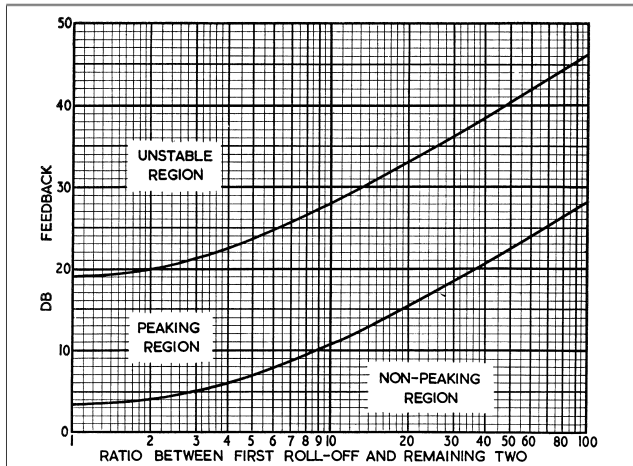


FIGURE 3: Limit chart for feedback loops in which three reactances contribute to the rolloff of response. The ratio is between the rolloff acting nearest the pass band of the amplifier, and two others about equal in cutoff frequency.

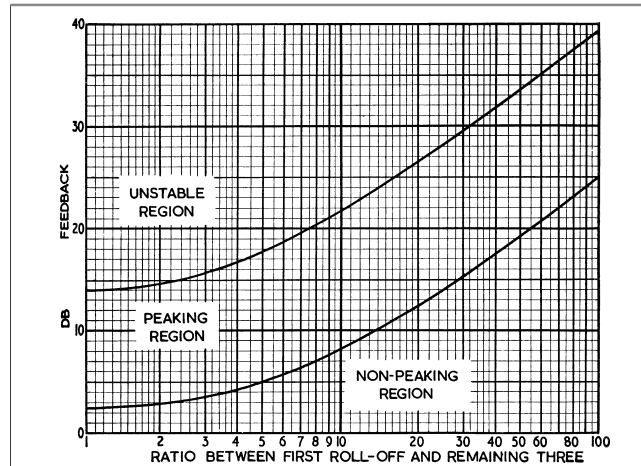


FIGURE 4: Limit chart for feedback loops in which four reactances contribute to the rolloff at one end of the response.

preset gain control R1, for which a suitable value would be 250k.

LOW-FREQUENCY RESPONSE OF INNER LOOP

Now we must tackle the question of suitable values of coupling and other capacitors. This is where the stability criterion and response factors of the feedback arrangement become important.

First we take the short-loop feedback; this includes, at the low-frequency end, the coupling capacitors C6 and C7 in the feedback loop. There are then two sets of reactor elements in this feedback loop. We want to keep the response of this section as flat as possible, and roll it off fairly sharply at the end of a band somewhat wider than the response band we ultimately require.

The charts in Fig. 2 are useful in the design of two-stage coupling arrangements with feedback. They give the response around the loop when the feedback is closed. To avoid any possibility of transient effects, the response should be not less than 6dB down on the scale on the left-hand side of the center line.

We are using a feedback ratio of 5:1, which represents 14dB. Aligning these two points, 14dB at the left, with 6dB in the center, we find that the rolloff ratio on the right-hand scale has to be almost 20. If C8 and C9 were not in the feedback loop—that is, if the output were taken across resistors R15 and R16 directly—then the rolloff would be 6dB down at a frequency determined by dividing the midway frequency, between the rolloffs given by C6 and C7 and their associated

resistances, by the factor 2.24 (found on the left-hand side of the left-hand scale, opposite 14dB).

But C8 and C9 are *in* the feedback loop, and their reactance is included in series with the resistances R15 and R16 in determining the output voltage. So, if the low-frequency rolloff provided by C8 and C9 is 20 times that provided by C6 and C7, the resultant loop response would be about 6dB down at a frequency 2.24 times that of the rolloff at C6 and C7. But at this frequency the reactance of C8 and C9 would be about 9.5 times the resistance values of R15 and R16, which means there would be a boost of almost 20dB, added to the loss of 6dB, producing a resultant peak of about 14dB at this frequency.

To avoid this effect it is necessary to have the rolloff provided by C8 and C9 operate at a frequency *lower* than that provided by C6 and C7. Then we shall be perfectly safe, and the effective rolloff frequency will be much lower than that without feedback. Therefore, we pick values of C6 and C7 to give a rolloff at 20cps (*cycles per second, which are now referred to as hertz.—Ed.*). With R18 and R19 at 330k, the reactance of C6 and C7 should be somewhere around 330k at 20cps. A suitable capacitor value is .025μF.

Now we need a value for C8 and C9 that will roll off at $\frac{1}{20}$ th of this frequency, or at 1cps. The reactance required is 82k; a capacitor to give a reactance of 82k at 1cps is 2μF. Small tabular electrolytics can be obtained with a capacitance of 2μF at a working voltage of 450V. These


should be quite satisfactory for C8 and C9. The signal-voltage swing at this point is 325V peak, so any leakage current is not likely to introduce noticeable noise in the circuit. The 14dB of feedback over this output loop will reduce the effective rolloff point of C6 and C7 by a ratio of 5:1, so that now the rolloff of these two stages will be 3dB at about 4cps.

To avoid unbalance, or phase shifts at the low-frequency end, C5 should roll off well below 4cps in conjunction with the 1MΩ grid resistor. A 0.25μF capacitor gives a reactance of 1MΩ at about 0.65cps. This should be quite satisfactory for this position in the circuit.

HIGH-FREQUENCY RESPONSE OF INNER LOOP

The high-frequency end is not so simple to evaluate in exact terms. We can only make a guess at it. The plate resistance of the 12AU7 is listed at 7,700Ω. This will be from each plate to ground, and the capacitance shunting this resistance will be that of the stray wiring, including the coupling capacitors C6 and C7, which are quite small physically, and the grid input capacitance of the 6L6s. This should not add more than about 50μF (*now pF*) altogether, which has a reactance of 7,700Ω at about 400kc (*kHz*).

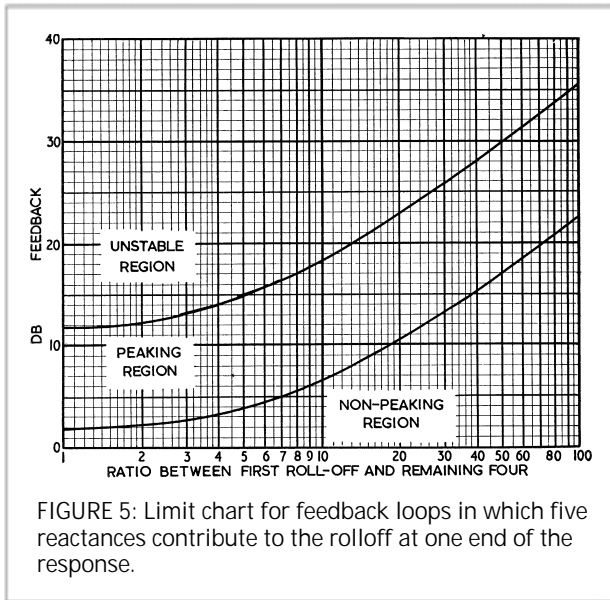To comply with the no-transient-distortion condition previously specified, we need to have a 20:1 ratio in high-frequency rolloff frequencies. In the output circuit, the 6L6 has a plate-to-plate load resistance of 9,000Ω, which takes the form of 2,250Ω from each plate to ground. The plate resistance will be



about ten times this value, or 22,500Ω per tube. Assuming the amplifier is correctly loaded with its 9,000Ω plate-to-plate, the impedance at each plate will be about 2,000Ω to ground, or 8,000Ω plate-to-plate. This should then be bypassed with a capacitor that will give a rolloff at 20kc. At 20kc, a reactance of 8,000Ω would be given by a .001μF capacitor, connected across the primary of the output transformer.

Without feedback this would give a rolloff of 3dB at 20kc. The effect of the feedback, with the staggered rolloff arrangement, is to increase the rolloff frequency to about 9.5 times 20kc for 6dB loss, or 190kc. There will then be no detectable loss at 20kc.

LOW-FREQUENCY RESPONSE, OUTER LOOP

We have the last two stages designed, complete with feedback, to give rolloffs of 3dB at 4cps and 6dB at 190kc. Now we can proceed to determine the circuit constants for the rest of the amplifier to suit the 20dB feedback applied overall.

The reactances contributing to low-frequency rolloff are the coupling capacitor C2, the coupling capacitor C4, the pair of coupling capacitors already considered, C6 and C7, and the primary inductance of the output transformer. Thus the main feedback loop has four reactance stages that contribute to low-frequency rolloff. This means we can use the limit chart of Fig. 4 to determine the ratio of rolloff frequencies to be used (Fig. 3 and 5 are similar charts for three and five reactance stages, respectively). These charts provide the ratio by which one cutoff frequency should be nearer the passband of the am-

plifier than the remaining ones, in order to determine the criterion of stability and also the point at which peaking begins to occur.

If we can make one of the RC networks have a rolloff frequency about 50 times higher than the remaining three, we shall almost avoid peaking completely, and have a very good stability margin. As we have already made the output end of the amplifier look like an arrangement with

a rolloff at 4cps, we can proceed to make the rest of the amplifier look like this, and arrange for one capacitor to roll off at 200cps.

The primary inductance of the output transformer should not show a loss of more than 3dB at 4cps at low levels, if it is not to distort at 20cps, because pentode tubes run into distortion quite quickly with elliptical loads. If a high-quality output transformer is being used to avoid this distortion, the inductance of the transformer should be satisfactory.

It remains to set the rolloff provided by C4 at cps also; a value of .08μF will provide a slight margin for error in tolerance.

Finally, we utilize C2 to provide the earlier rolloff at 200cps. C2 should then be .0015μF, which gives a reactance of 520k at 200cps, again allowing a slight margin for tolerance error.

Does not this mean the entire amplifier will now roll off at 200cps? The feedback provided is 20dB, so this will extend

the rolloff downwards, by a factor of 10:1, to 20cps. The rolloff at 20cps will be considerably sharpened by the fact that it is not a single-reactance rolloff, but that by now the other three reactances around the loop are contributing. It is a good feature to have a sharp rolloff below 20cps to filter out rumble and other undesirable effects.


The 12AX7 stage will give an output of 32V peak successfully. The signal handled by the first tube section is normally only 52 × 4mV peak, a little more than 200mV. When the feedback disappears, because of the reactance of C2 at 20cps, the voltage swing at the plate of the first half of the 12AX7 will rise to about ten times this value, or a little over 2V, which is still well within the voltage-handling margin of the tube.

We can see now why C2 is the best place to put the smaller coupling capacitor. If C4 were used for this extra rolloff purpose, the signal amplitude at the plate of the second half of the 12AX7 would also be multiplied by ten times at the bottom end of the frequency band, and there is not enough margin to allow for this. The signal there is already 11V peak; ten times this would raise the signal to 110V peak, which the 12AX7 should certainly not be expected to deliver.

HIGH-FREQUENCY RESPONSE, OUTER LOOP

Applying the same reasoning to the high-frequency rolloff, there are four high-impedance points that will be shunted by different capacitance values: the first and second plates of the 12AX7, each plate of the 12AU7, which is in push-pull, and the plates of the 6L6s, also in push-pull.

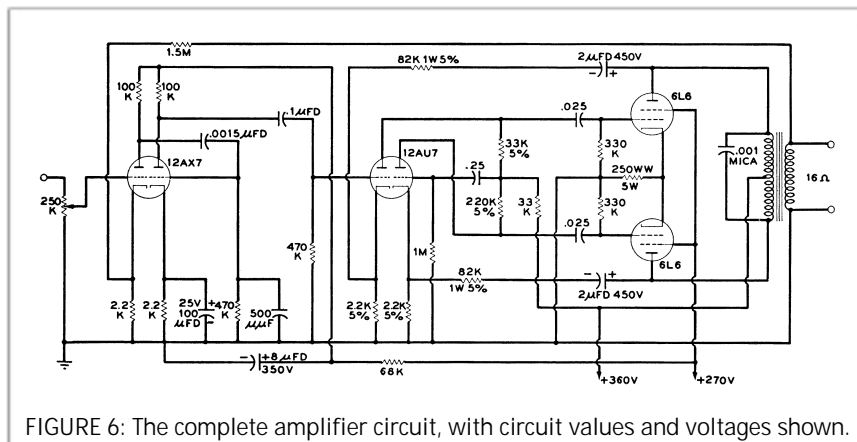The effective rolloffs of the last two have been modified by the inner-loop feedback arrangement so that both are effectively at 190kc. The plate resistance



of the 12AX7 is quoted at 62.5k, but for a higher operating level than is used here. An estimate of 100k should be safe for this condition. The total capacitance in the grid circuit of the first 12AU7, with 14dB feedback effective, should not be more than about 10 μ F, which has a reactance of 100k at about 160kc. This is reasonably consistent with the pattern so far.

Applying the same method as that used at the low-frequency end, the plate circuit of the first half of the 12AX7 should have a rolloff at about $\frac{1}{50}$ th of 160kc (taking the lower figure), or 3.2kc. A capacitor to give a reactance of 100k at 3.2kc is 500 μ F; this we put across the second-stage grid resistor. With 20dB feedback, the rolloff frequency will be pushed out to around 32kc.

We now have an amplifier with a response sensibly flat from 20cps to beyond 20kc, and with a total of 34dB feedback in the two loops, which is fully effective from 200cps to 3,200cps. Beyond these frequencies, the amount of feedback available rolls off slightly, but there is still not less than 14dB feedback over the output stage to the extreme limits of the band. As we have taken careful steps to see that the distortion in the absence of feedback is at a minimum, the amplifier should give very good performance.

POWER SUPPLY COMPONENTS

The only components we now have left to specify are those in the power supply. R6 and C3 must reduce a supply voltage of 270 (the same as that for the output-tube screen grids), and provide some decoupling. The B+ voltage we need for the 12AX7 tube is 180V, so we can allow a 90V drop in R6 at a total current drain of 1.2mA (0.6mA for each tube section). R6 is accordingly set at 75k. In practice, 68k will serve, because the voltage here is not critical. C3 can be 8 μ F, 350V working; this will give a reactance of less than 20k down to 1cps, and hence cannot interfere with the rolloff frequencies we have just calculated.

The cathode bypass capacitor C1, which is across 2.2k, should be not less than 100 μ F, 25V working. This will give a reactance of less than 1,600 Ω down to a frequency of 1cps.

For the B+ supply, we need a maximum of 360V at a total current drain of about 125mA. This can be provided by a power transformer with a 350-0-350 secondary winding, a 5U4 rectifier, and a capacitor-choke-capacitor filter, the design of which has been dealt with elsewhere in Joseph Marshall's "Practical

Audio Design" (*Audiocraft*, Jan., Feb., Mar., 1956).

This article has discussed the complete design of a feedback amplifier, and has introduced all the factors to be considered, as painlessly as possible. From this it will be seen that, taken step by step, there is nothing very difficult about the design of such an amplifier. In the next article of this series, we shall take a step further and consider special kinds of output arrangements and the design factors involved in getting the best out of these circuits. ❖