

Snubber Circuits

- A. Overview of Snubber Circuits
- B. Diode Snubbers
- C. Turn-off Snubbers
- D. Overvoltage Snubbers
- E. Turn-on Snubbers
- F. Thyristor Snubbers

William P. Robbins
Professor
Dept. of Electrical Engineering
University of Minnesota
200 Union St. SE.
Minneapolis, MN 555455

Copyright 1997

Function of Snubber Circuits

- Protect semiconductor devices by:
 - Limiting device voltages during turn-off transients
 - Limiting device currents during turn-on transients
 - Limiting the rate-of-rise ($\frac{di}{dt}$) of currents through the semiconductor device at device turn-on
 - Limiting the rate-of-rise ($\frac{dv}{dt}$) of voltages across the semiconductor device at device turn-off
 - Shaping the switching trajectory of the device as it turns on/off

Types of Snubber Circuits

1. Unpolarized series R-C snubbers

- Used to protect diodes and thyristors


2. Polarized R-C snubbers

- Used as turn-off snubbers to shape the turn-on switching trajectory of controlled switches.
- Used as overvoltage snubbers to clamp voltages applied to controlled switches to safe values.
- Limit $\frac{dv}{dt}$ during device turn-off


3. Polarized L-R snubbers

- Used as turn-on snubbers to shape the turn-off switching trajectory of controlled switches.
- Limit $\frac{di}{dt}$ during device turn-on

Need for Diode Snubber Circuit


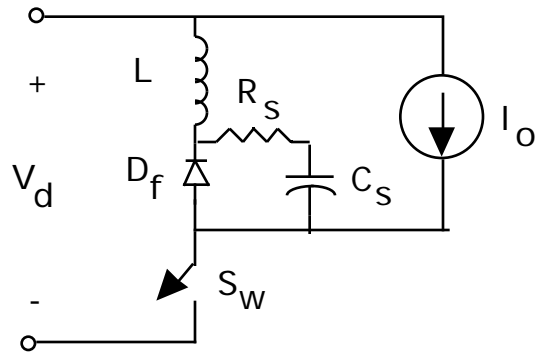


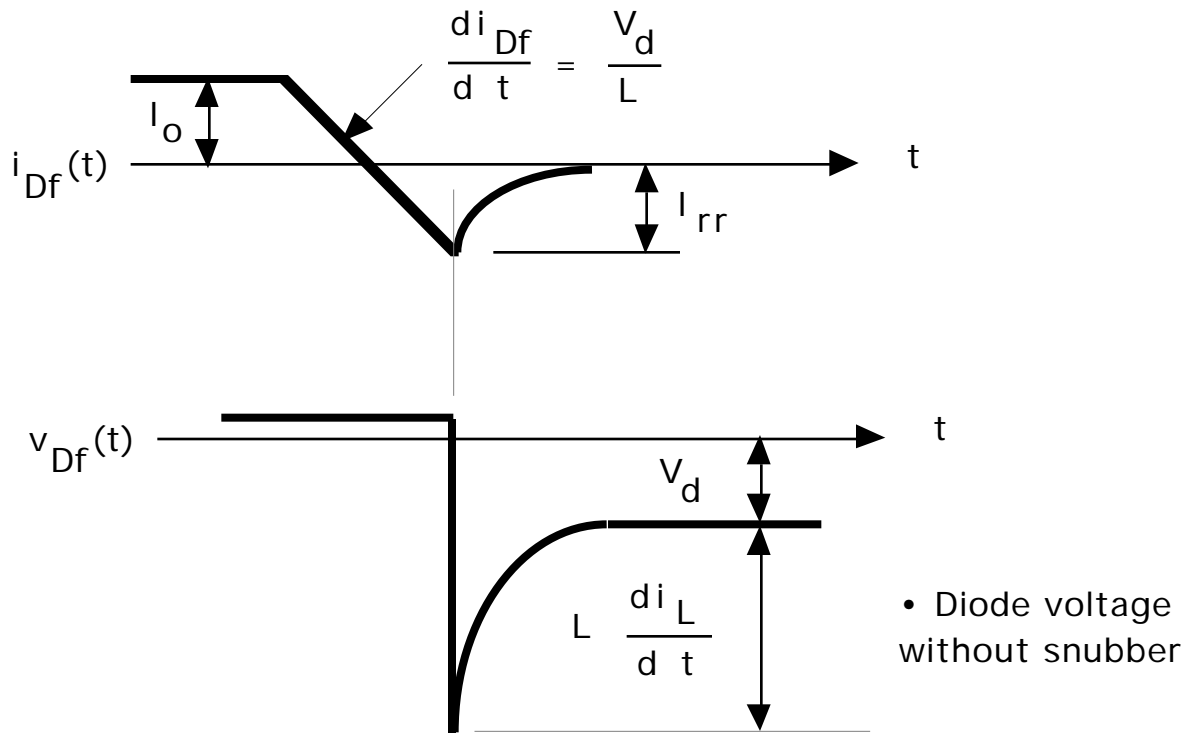- L = stray inductance
- S_W closes at $t = 0$
- $R_S - C_S$ = snubber circuit




- Diode breakdown if $V_d + L \frac{di_L}{dt} > BV_{BD}$

Equivalent Circuits for Diode Snubber

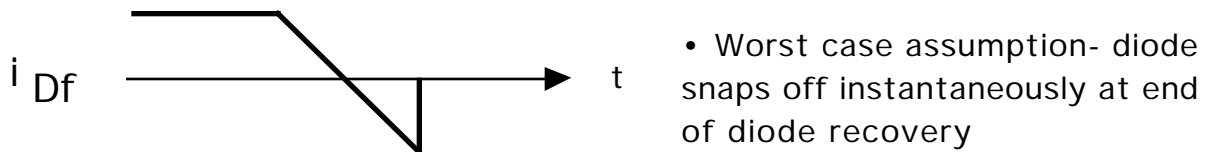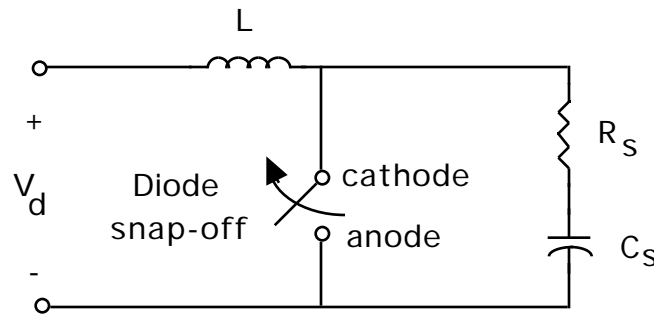

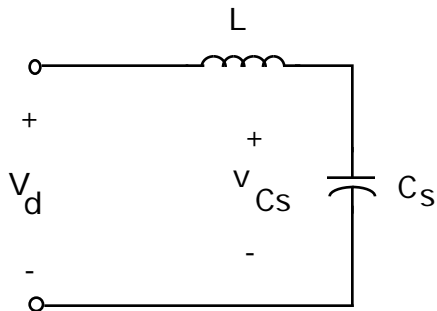- Simplified snubber - the capacitive snubber



- $R_s = 0$
- $v_{C_s} = -v_{Df}$


- Governing equation -
$$\frac{d^2 v_{C_s}}{dt^2} + \frac{v_{C_s}}{L C_s} = \frac{V_d}{L C_s}$$
- Boundary conditions - $v_{C_s}(0^+) = 0$ and $i_L(0^+) = I_{rr}$

Performance of Capacitive Snubber

- $$v_{Cs}(t) = V_d - V_d \cos(\omega t) + V_d \sqrt{\frac{C_{base}}{C_s}} \sin(\omega t)$$


- $$\omega = \frac{1}{\sqrt{L C_s}} \quad ; \quad C_{base} = L \frac{I_{rr}^2}{V_d^2}$$

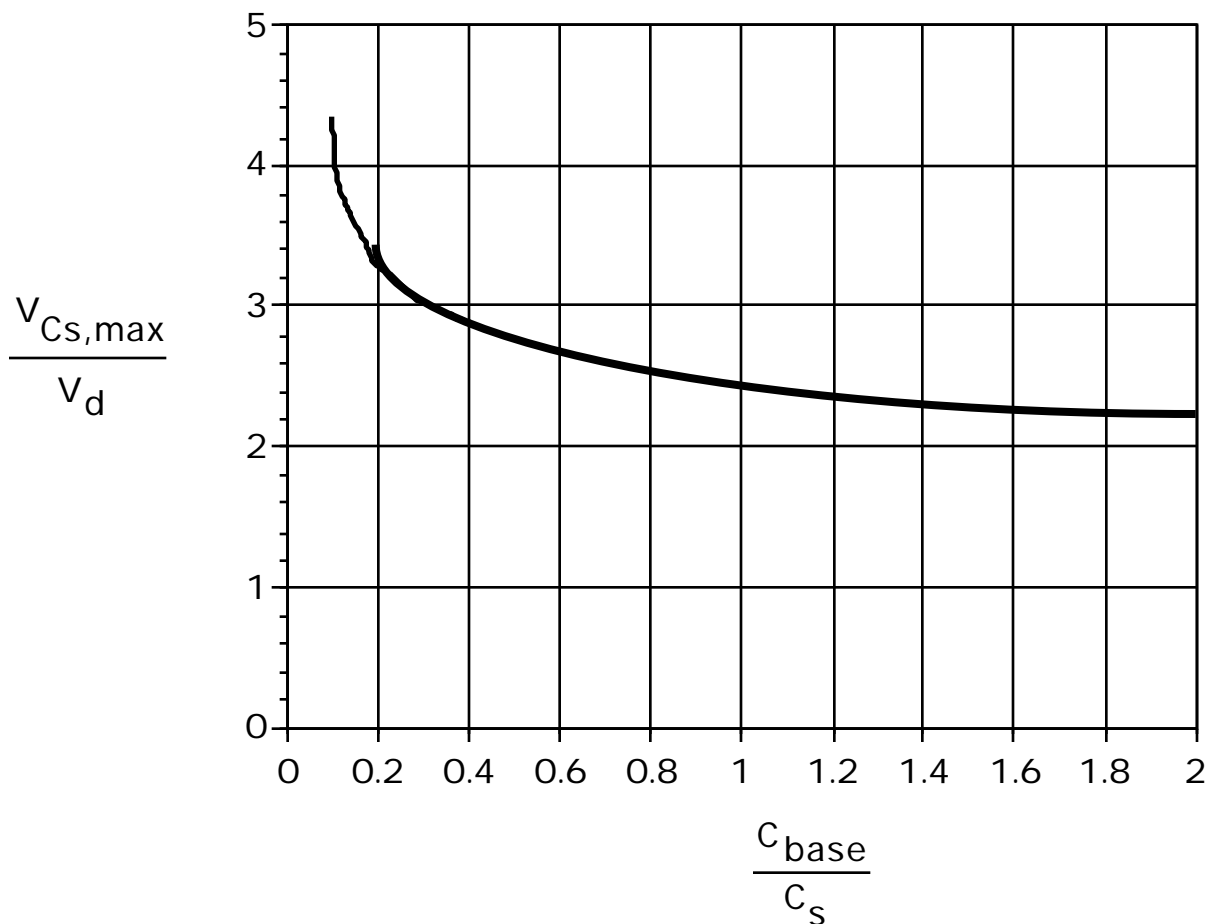- $$V_{Cs,max} = V_d \left(1 + \sqrt{1 + \frac{C_{base}}{C_s}} \right)$$



Effect of Adding Snubber Resistance

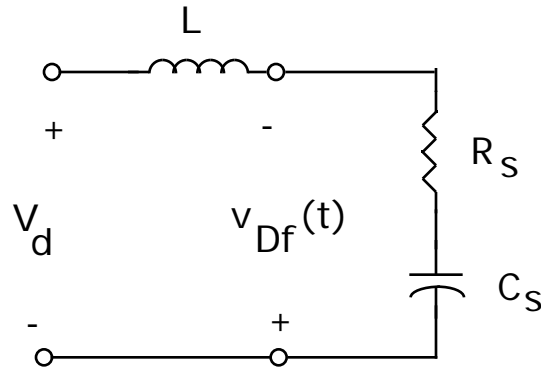- Equivalent circuit with snubber resistance R_S



- Governing equation $L C_S \frac{d^2 v_{Df}}{dt^2} + R_S C_S \frac{dv_{Df}}{dt} + v_{Df} = -V_d$

- Boundary conditions

$$v_{Df}(0^+) = -I_{rr} R_S \quad \text{and} \quad \frac{dv_{Df}(0^+)}{dt} = -\frac{I_{rr}}{C_S} - \frac{R_S V_d}{L} + \frac{I_{rr} R_S^2}{L}$$

- Solution for $v_{Df}(t)$

$$v_{Df}(t) = -V_d - V_d e^{-\alpha t} \sqrt{\frac{C_{base}}{C_S}} \sin(\omega t - \phi)$$

$$\alpha = \frac{R_S}{2L} \sqrt{1 - \frac{R_S^2}{4L^2}} \quad ; \quad \omega = \frac{1}{\sqrt{L C_S}} \quad ; \quad \phi = \frac{R_S}{2L}$$

$$\tan(\phi) = -\frac{R_b}{aL} - \frac{1}{a} \quad ; \quad \tan(\phi) = \frac{1}{a} \quad ; \quad R_{base} = \frac{V_d}{I_{rr}} \quad , \quad C_{base} = \frac{L}{(V_d/I_{rr})^2}$$

Performance of R-C Snubber


- At $t = t_m$ $v_{Df}(t) = V_{max}$

- $$t_m = \frac{\tan^{-1}(a/\omega)}{a} + \frac{L}{a} \quad 0$$


- $$\frac{V_{max}}{V_d} = 1 + \sqrt{1 + C_N^{-1} - R_N} \exp(-t_m)$$

- $$C_N = \frac{C_s}{C_{base}} \quad \text{and} \quad R_N = \frac{R_s}{R_{base}}$$

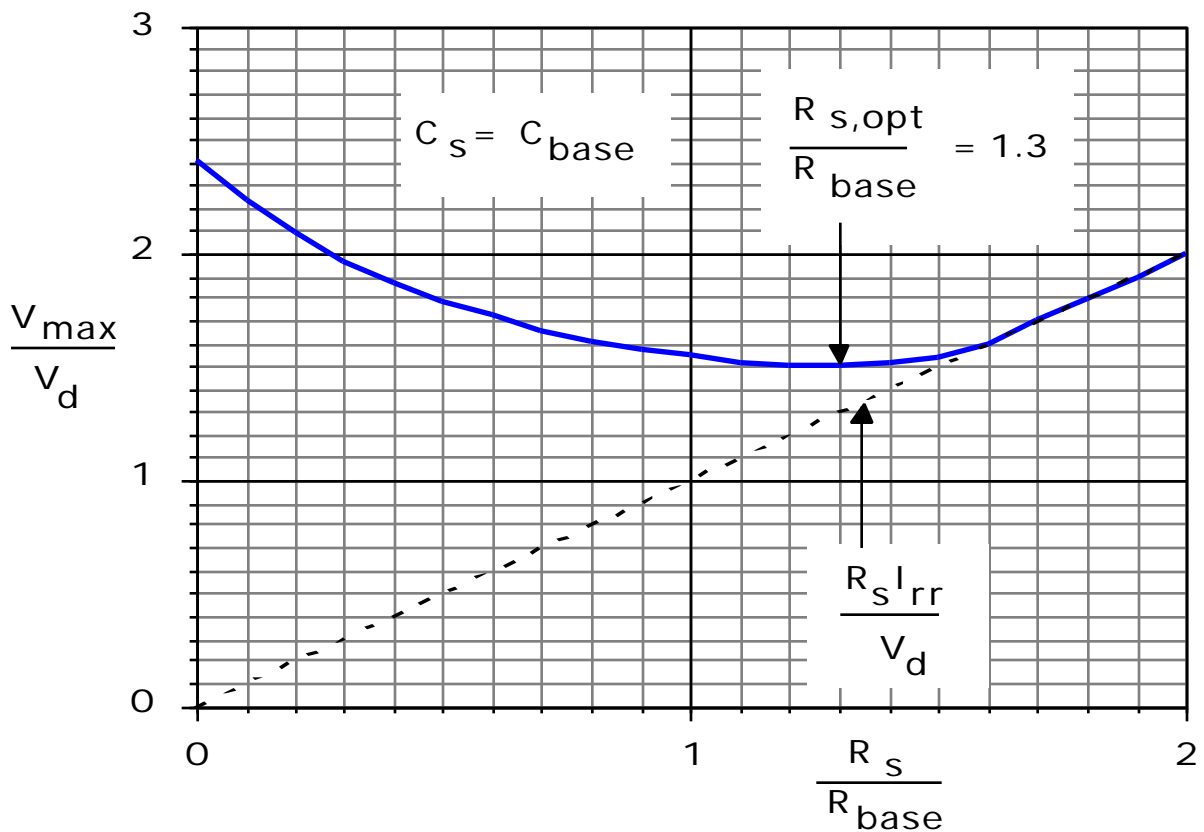
- $$C_{base} = \frac{L_s I_{rr}^2}{V_d^2} \quad \text{and} \quad R_{base} = \frac{V_d}{I_{rr}}$$



Diode Snubber Design Nomogram


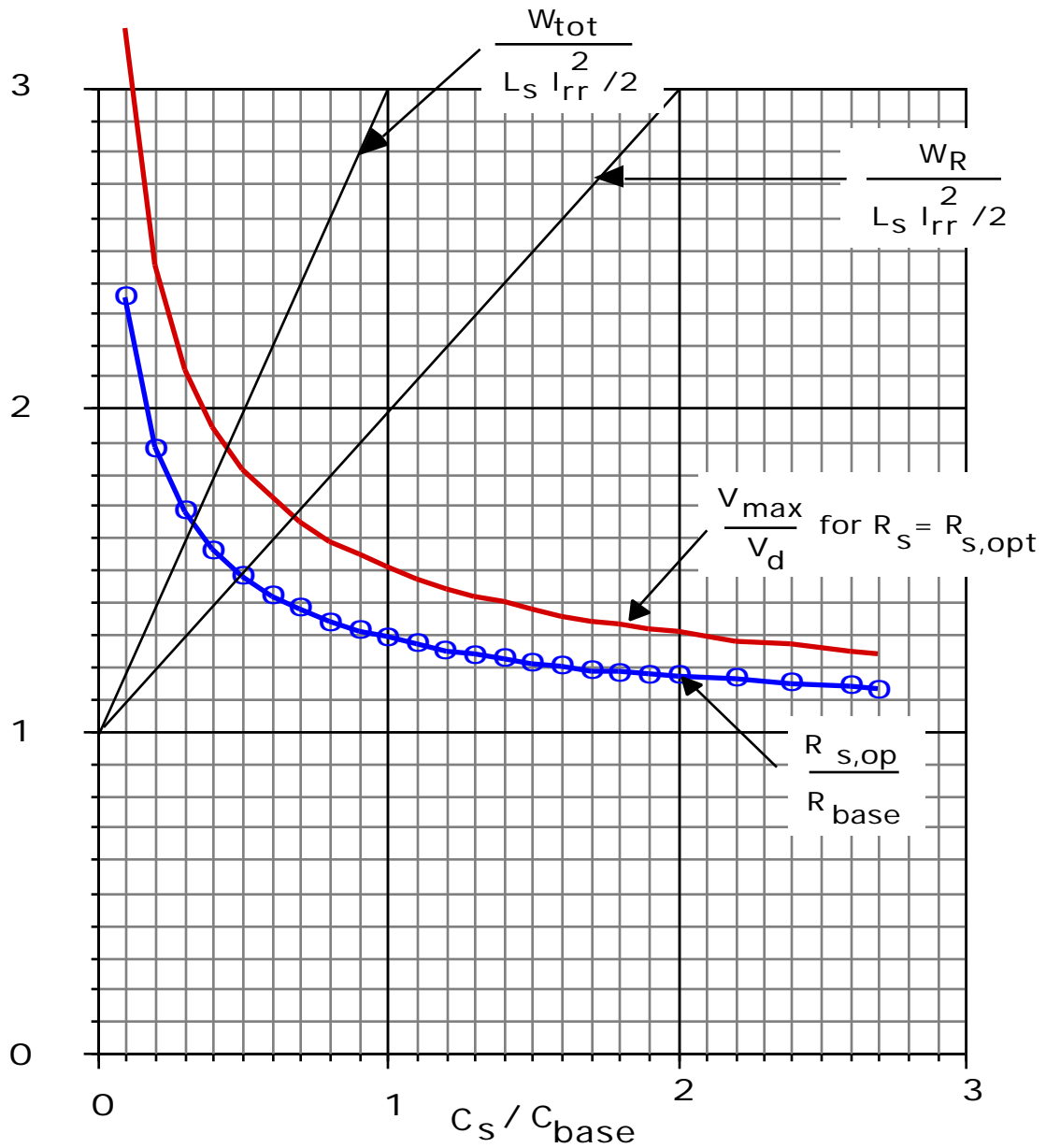


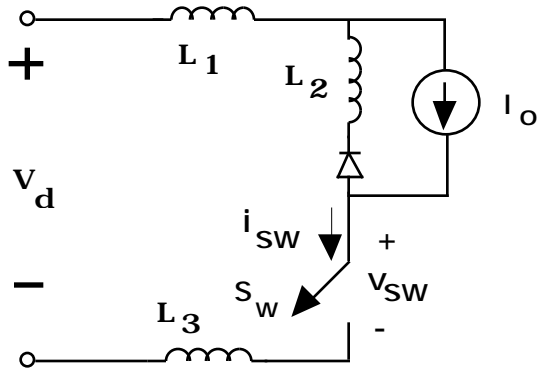Need for Snubbers with Controlled Switches



• $L_1, L_2, L_3 =$ stray inductances

• $L_\sigma = L_1 + L_2 + L_3$

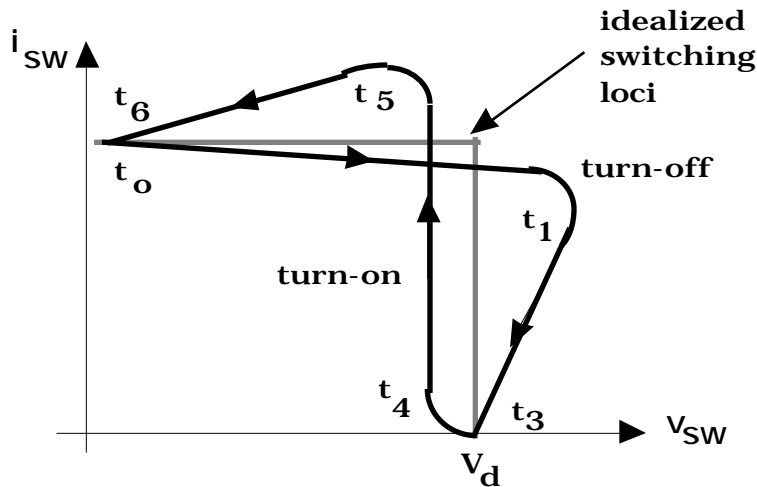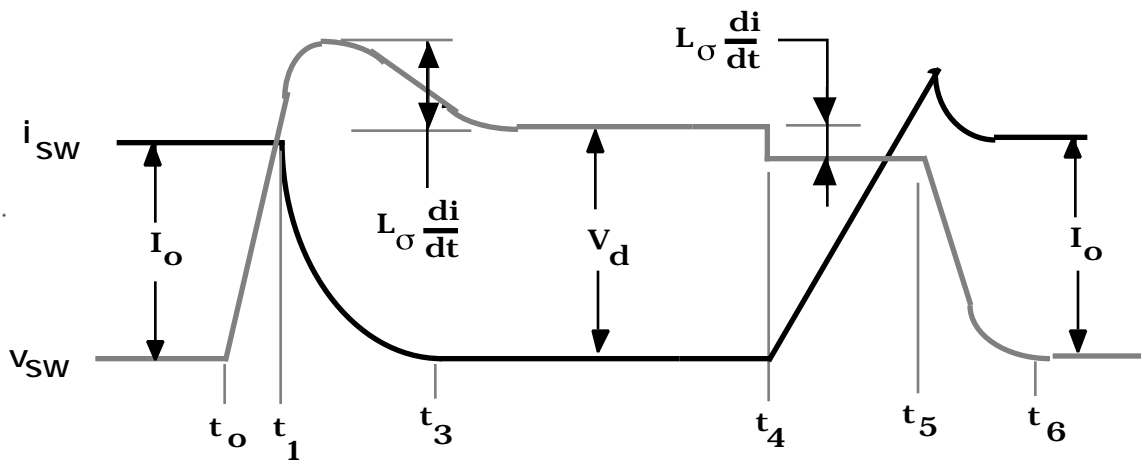


• Overvoltage at turn-off due to stray inductance


• Overcurrent at turn-on due to diode reverse recovery

Turn-on Snubber for Controlled Switches

- Circuit configuration

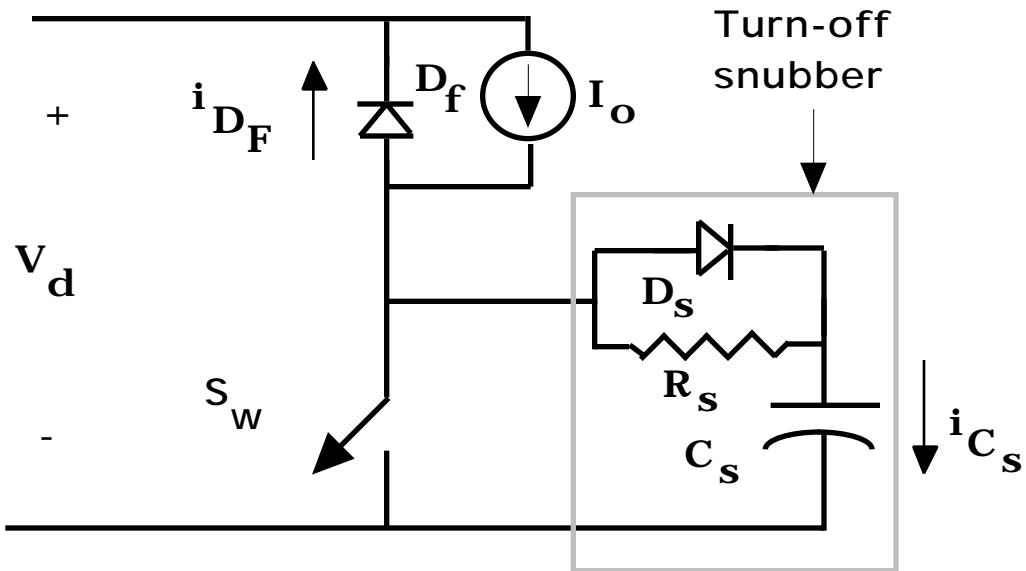

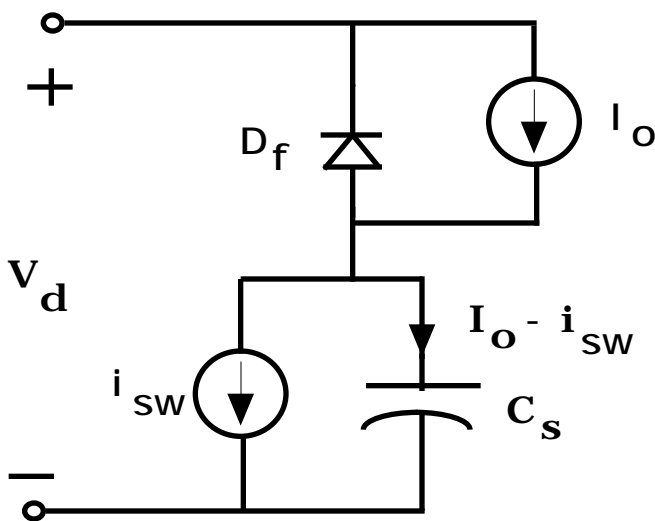- Equivalent circuit during switch turn-off




- Assumptions

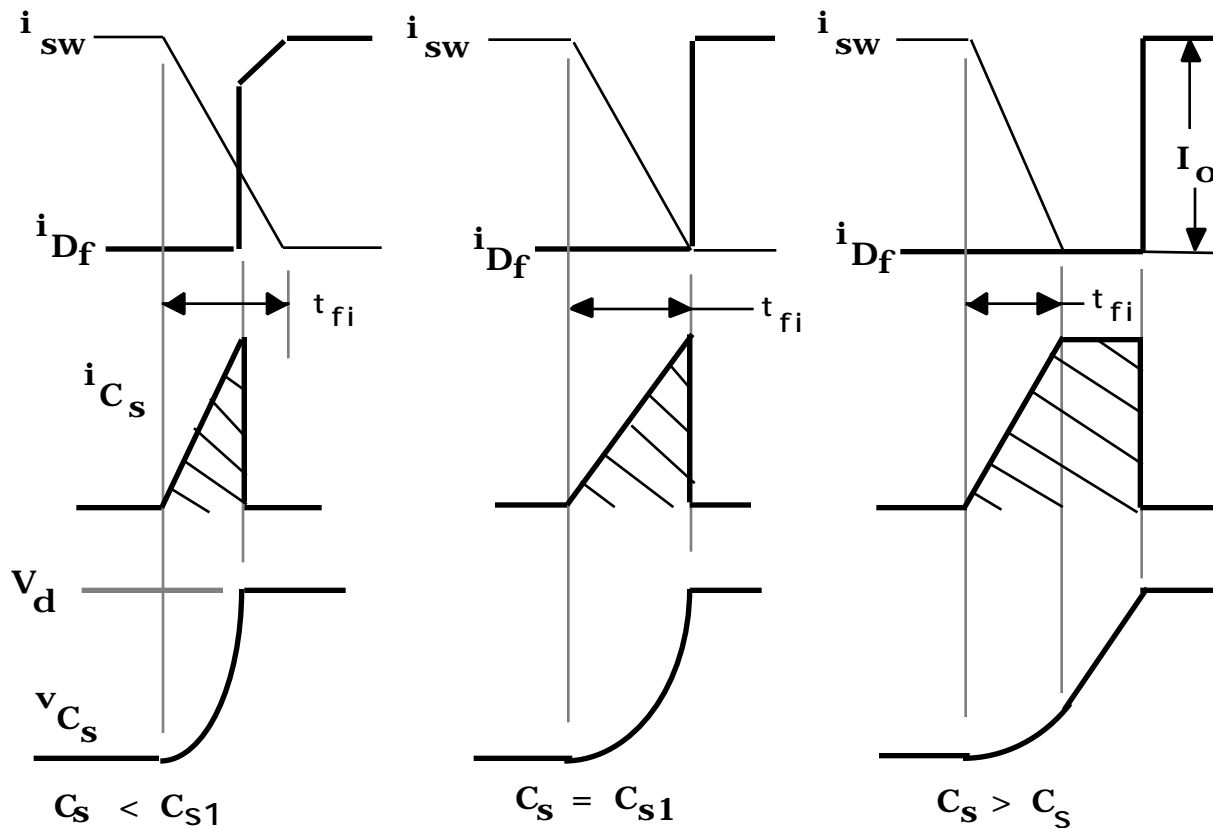
1. No stray inductance.
2. $i_{sw}(t) = I_o(1 - t/t_{fi})$
3. $i_{sw}(t)$ unaffected by snubber circuit.

Turn-off Snubber Operation


- Capacitor voltage and current for $0 < t < t_{fi}$
 - $i_{C_s}(t) = \frac{I_o t}{t_{fi}}$ and $v_{C_s}(t) = \frac{I_o t^2}{2C_s t_{fi}}$
- For $C_s = C_{s1}$, $v_{C_s} = V_d$ at $t = t_{fi}$ yielding $C_{s1} = \frac{I_o t_{fi}}{2V_d}$
- Circuit waveforms for varying values of C_s



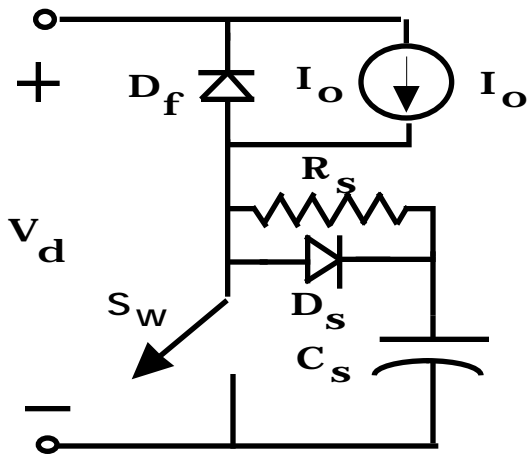Benefits of Snubber Resistance at S_W Turn-on




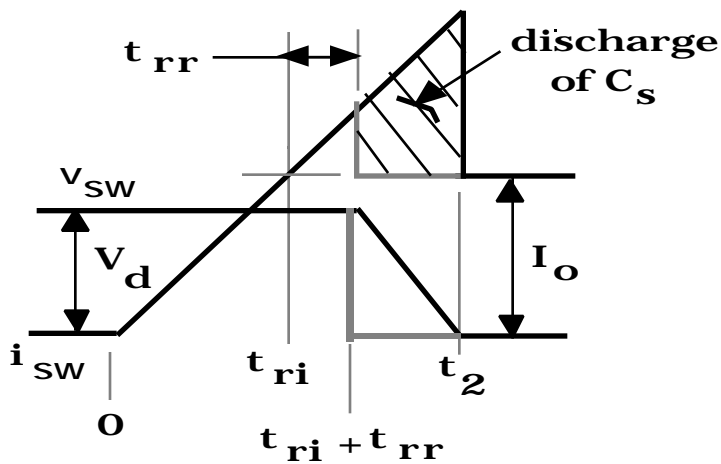- D_S shorts out R_S during S_W turn-off.
- During S_W turn-on, D_S reverse-biased and C_S discharges thru R_S .




- Turn-on with $R_S = 0$
- Energy stored on C_S dissipated in S_W .
- Extra energy dissipation in S_W because of lengthened voltage fall time.

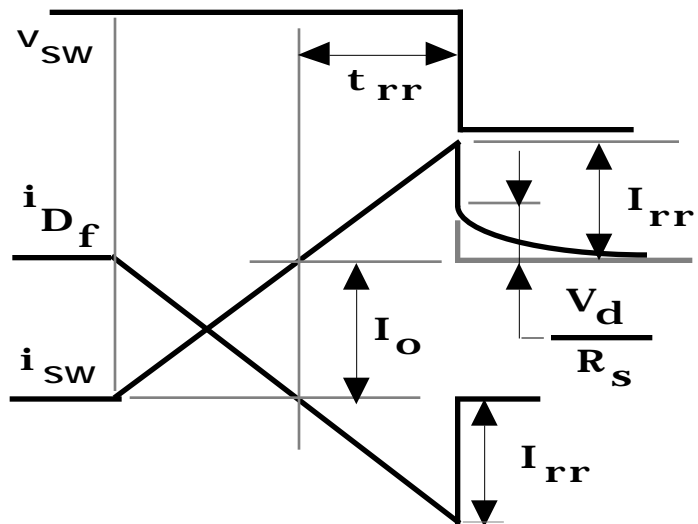- Turn-on with $R_S > 0$
- Energy stored on C_S dissipated in R_S rather than in S_W .
- Voltage fall time kept quite short.




Effect of Snubber Capacitance

- Switching trajectory

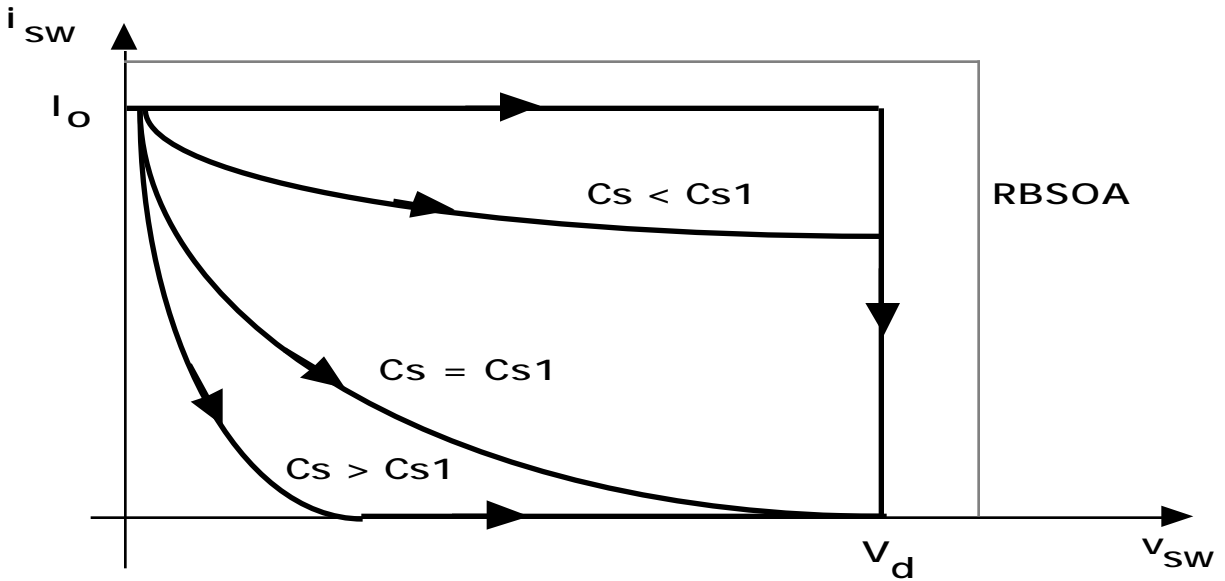

- Energy dissipation

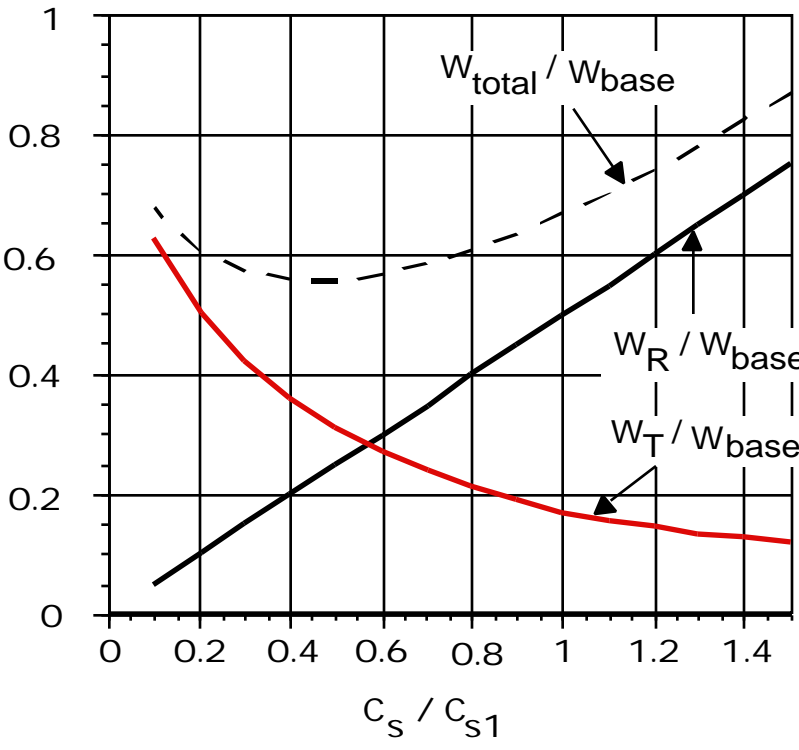

W_R = dissipation in resistor

W_T = dissipation in switch S_w

$$C_{s1} = \frac{I_o t_{fi}}{2V_d}$$

$$W_{total} = W_R + W_T$$


$$W_{base} = 0.5 V_d I_o t_{fi}$$

Turn-off Snubber Design Procedure


- Selection of C_S
 - Minimize energy dissipation (W_T) in BJT at turn-on
 - Minimize $W_R + W_T$
 - Keep switching locus within RBSOA
 - Reasonable value is $C_S = C_{S1}$
- Selection of R_S
 - Limit $i_{cap}(0^+) = \frac{V_d}{R_S} < I_{rr}$
 - Usually designer specifies $I_{rr} < 0.2 I_O$ so
$$\frac{V_d}{R_S} = 0.2 I_O$$
- Snubber recovery time (BJT in on-state)
 - Capacitor voltage = $V_d \exp(-t/R_S C_S)$
 - Time for v_{C_S} to drop to $0.1V_d$ is $2.3 R_S C_S$
 - BJT must remain on for a time of $2.3 R_S C_S$

Overvoltage Snubber for Controlled Switches

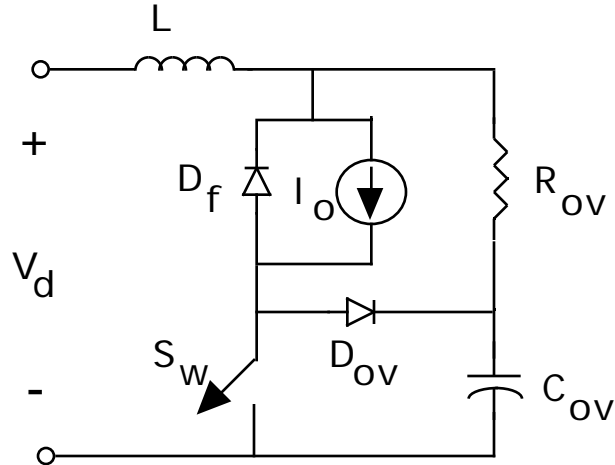- Circuit configuration - D_{OV} , R_{OV} , and C_{OV} form overvoltage snubber



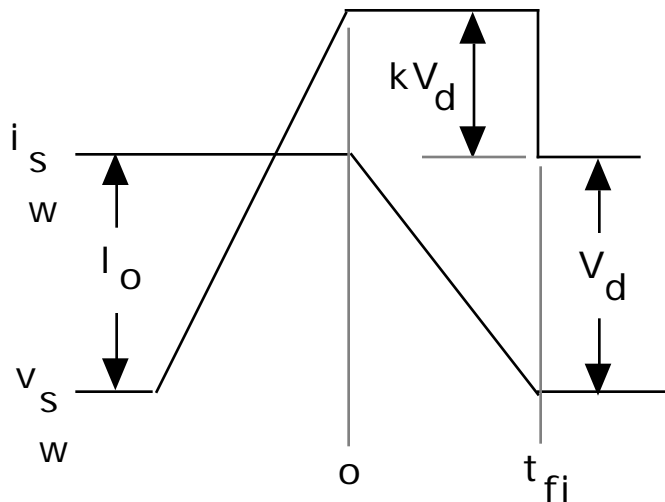- Overvoltage snubber limits magnitude of voltage developed across S_W as it turns off.
- Switch S_W waveforms without overvoltage snubber
 - t_{fi} = switch current fall time ; kV_d = overvoltage on S_W




$$kV_d = L \frac{di_L}{dt} = L \frac{I_o}{t_{fi}}$$

$$L = \frac{kV_d t_{fi}}{I_o}$$


Operation of Overvoltage Snubber

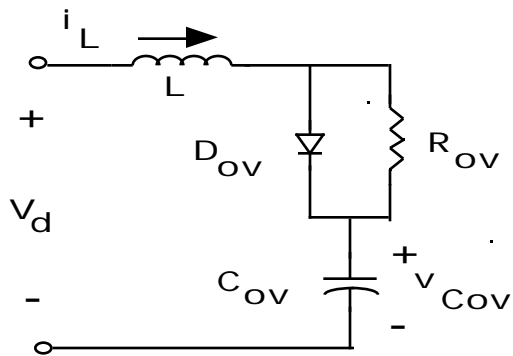- D_{OV}, C_{OV} provide alternate path for inductor current as S_W turns off.
 - Switch current can fall to zero much faster than L current.
- D_f forced to be on (approximating a short ckt) by I_O after S_W is off.
- Equivalent circuit after turn-off of S_W .



- D_{OV} on for $0 < t < \frac{\sqrt{L C_{OV}}}{2}$

- $t_{fi} \ll \frac{\sqrt{L C_{OV}}}{2}$

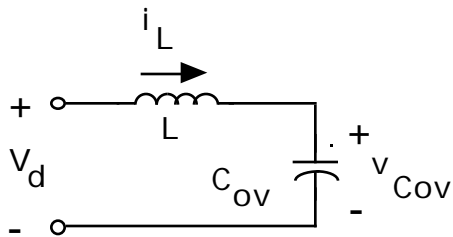


- Equivalent circuit while inductor current decays to zero

$$v_{C_{OV}}(0^+) = V_d \quad i_L(0^+) = I_O$$

$$i_L(t) = I_O \cos\left[\frac{t}{\sqrt{L C_{OV}}}\right]$$

Charge-up of C_{OV} from L

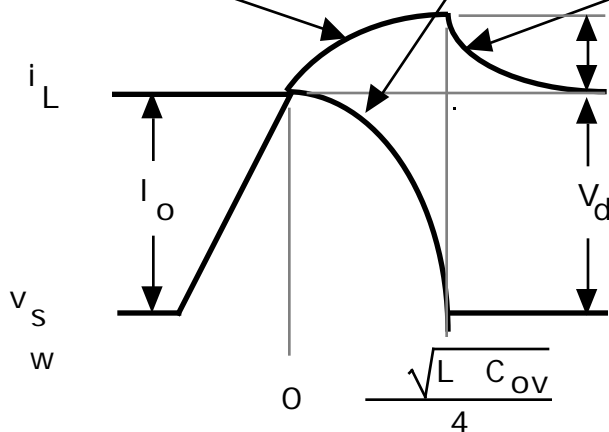Discharge of C_{OV} thru R_{OV} with time constant $R_{OV} C_{OV}$



- Energy transfer from L to C_{OV}


$$\frac{C_{OV} (V_{SW,max})^2}{2} = \frac{L (I_O)^2}{2}$$

Overvoltage Snubber Design


- $C_{OV} = \frac{L_S I_o^2}{(v_{sw,max})^2}$
- Limit $v_{sw,max}$ to $0.1V_d$
- Using $L_S = \frac{kV_d t_{fi}}{I_o}$ in equation for C_{OV} yields
 - $C_{OV} = \frac{kV_d t_{fi} I_o^2}{I_o (0.1V_d)^2} = \frac{100k t_{fi} I_o}{V_d^2}$
 - $C_{OV} = 200 C_{S1}$ where $C_{S1} = \frac{t_{fi} I_o}{2V_d}$ which is used in turn-off snubber
- Recovery time of C_{OV} ($2.3R_{OV}C_{OV}$) must be less than off-time duration, t_{off} , of the switch Sw.
 - $R_{OV} = \frac{t_{off}}{2.3 C_{OV}}$

Turn-on Snubber Circuit

- Circuit topology

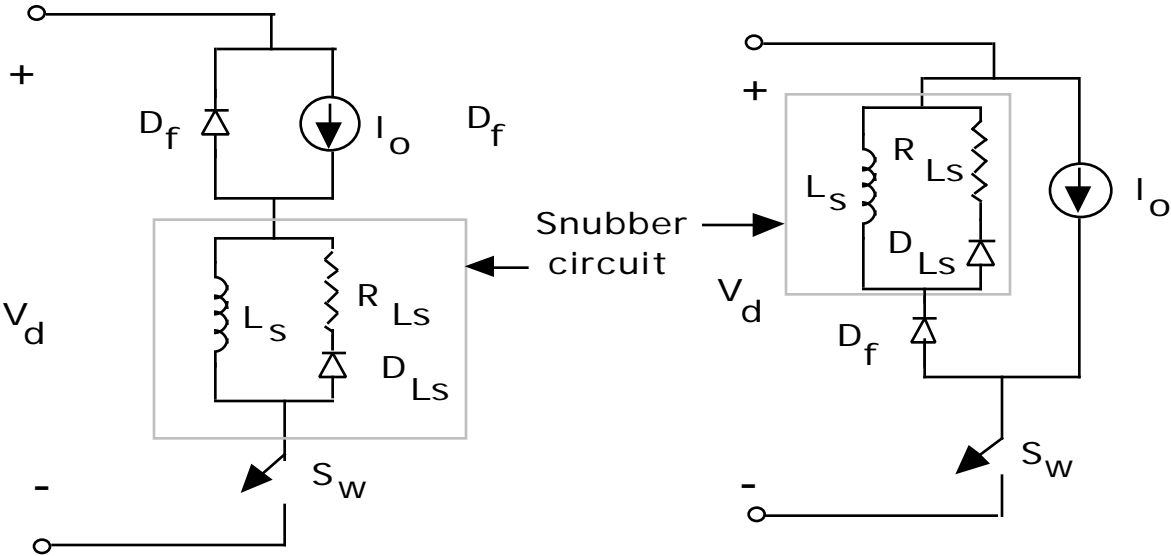


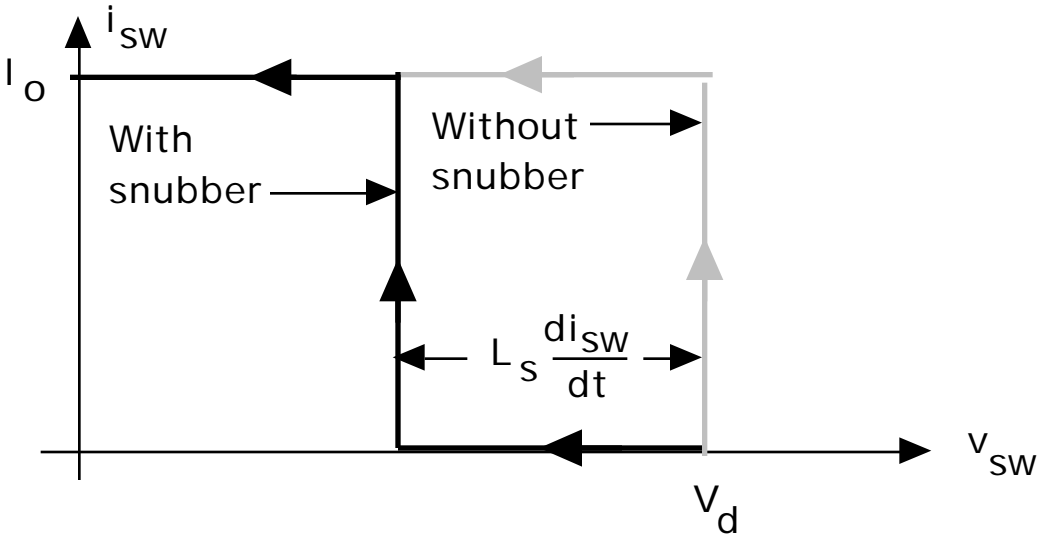- Circuit reduces V_{sw} as switch S_w turns on. Voltage drop $L_s \frac{di_{sw}}{dt}$ provides the voltage reduction.
- Switching trajectories with and without turn-on snubber.



Turn-on Snubber Operating Waveforms

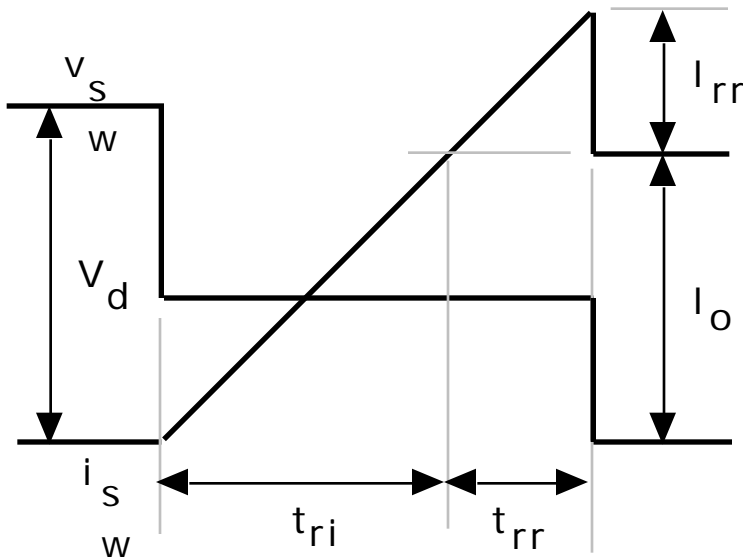
- Small values of snubber inductance ($L_S < L_{S1}$)



- $\frac{di_{sw}}{dt}$ controlled by switch S_w and drive circuit.

- $$v_{sw} = \frac{L_S I_o}{t_{ri}}$$

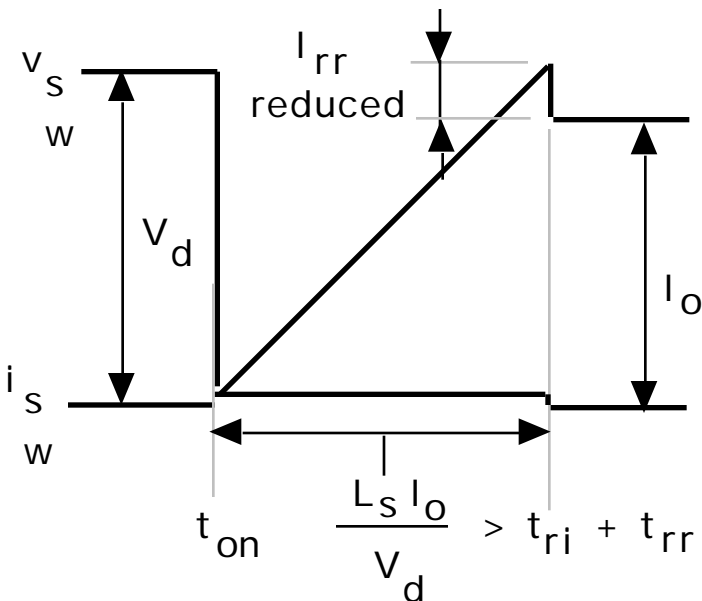- Large values of snubber inductance ($L_S > L_{S1}$).




- $\frac{di_{sw}}{dt}$ limited by circuit
to $\frac{V_d}{L_S} < \frac{I_o}{t_{ri}}$


- $$L_{S1} = \frac{V_d t_{ri}}{I_o}$$

- I_{rr} reduced when $L_S > L_{S1}$ because I_{rr} proportional to $\sqrt{\frac{di_{sw}}{dt}}$

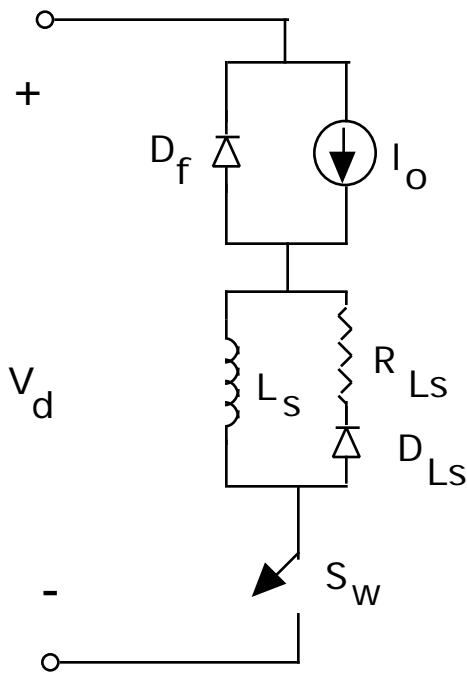Turn-on Snubber Recovery at Switch Turn-off



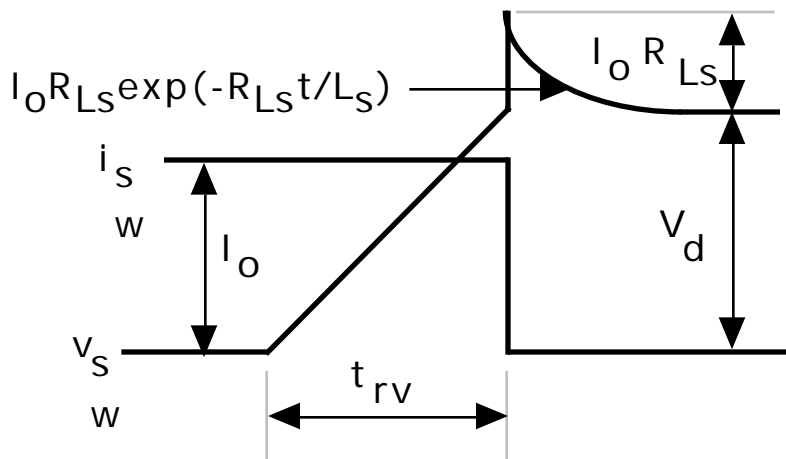- Assume switch current fall time $t_{ri} = 0$.
- Inductor current must discharge thru D_{LS} - R_{LS} series segment.




- Switch waveforms at turn-off with turn-on snubber in circuit.

- Overvoltage smaller if t_{fi} smaller.
- Time of $2.3 L_S/R_{L_S}$ required for inductor current to decay to $0.1 I_o$
- Off-time of switch must be $> 2.3 L_S/R_{L_S}$


Turn-on Snubber Design Trade-offs

- Selection of inductor L_S
 - Larger L_S decreases energy dissipation in switch at turn-on
 - $W_{SW} = W_B (1 + I_{rr}/I_O)^2 [1 - L_S/L_{S1}]$
 - $W_B = V_d I_O t_{fi}/2$ and $L_{S1} = V_d t_{fi}/I_O$
 - $L_S > L_{S1}$ $W_{SW} = 0$
 - Larger L_S increases energy dissipation in R_{LS}
 - $W_R = W_B L_S / L_{S1}$
 - $L_S > L_{S1}$ reduces magnitude of reverse recovery current I_{rr}
 - Inductor must carry current I_O when switch is on - makes inductor expensive and hence turn-on snubber seldom used
- Selection of resistor R_{LS}
 - Smaller values of R_{LS} reduce switch overvoltage $I_O R_{LS}$ at turn-off
 - Limiting overvoltage to $0.1V_d$ yields $R_{LS} = 0.1 V_d/I_O$
 - Larger values of R_{LS} shortens minimum switch off-time of $2.3 L_S/R_{LS}$

Thyristor Snubber Circuit

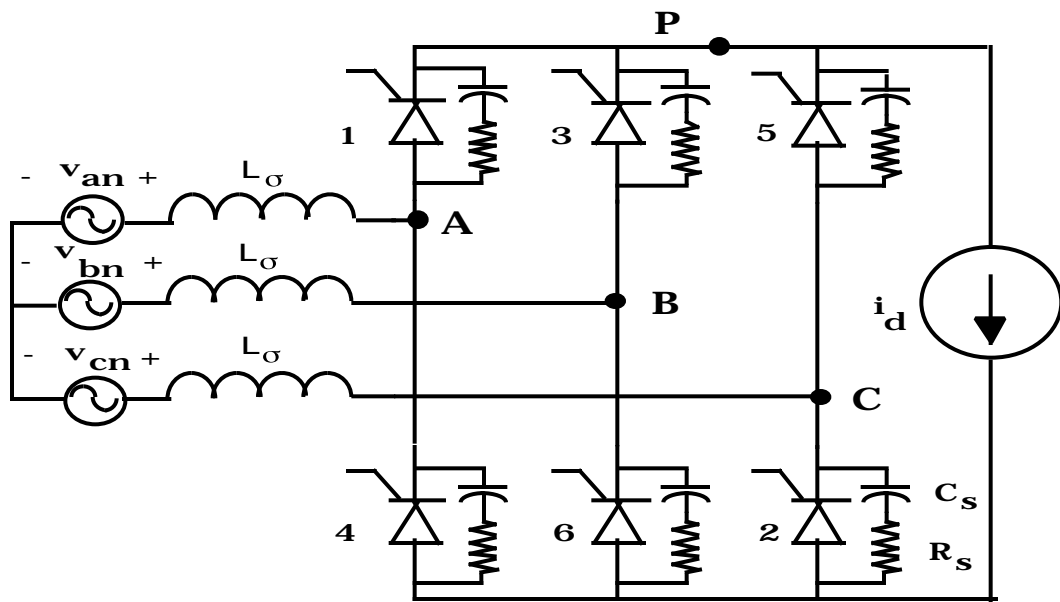

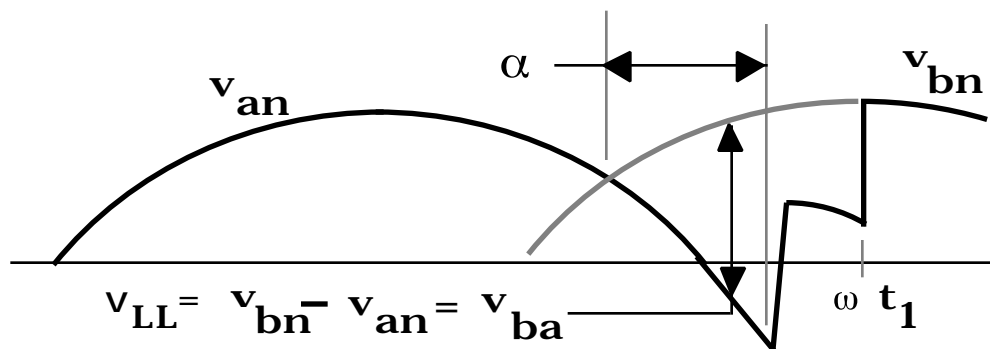
- $v_{an}(t) = V_s \sin(\omega t)$, $v_{bn}(t) = V_s \sin(\omega t - 120^\circ)$, $v_{cn}(t) = V_s \sin(\omega t - 240^\circ)$
- Phase-to-neutral waveforms



- $v_{LL}(t) = \sqrt{3} V_s \sin(\omega t - 60^\circ)$
- Maximum rms line-to-line voltage $V_{LL} = \sqrt{\frac{3}{2}} V_s$

Equivalent Circuit for SCR Snubber Calculations

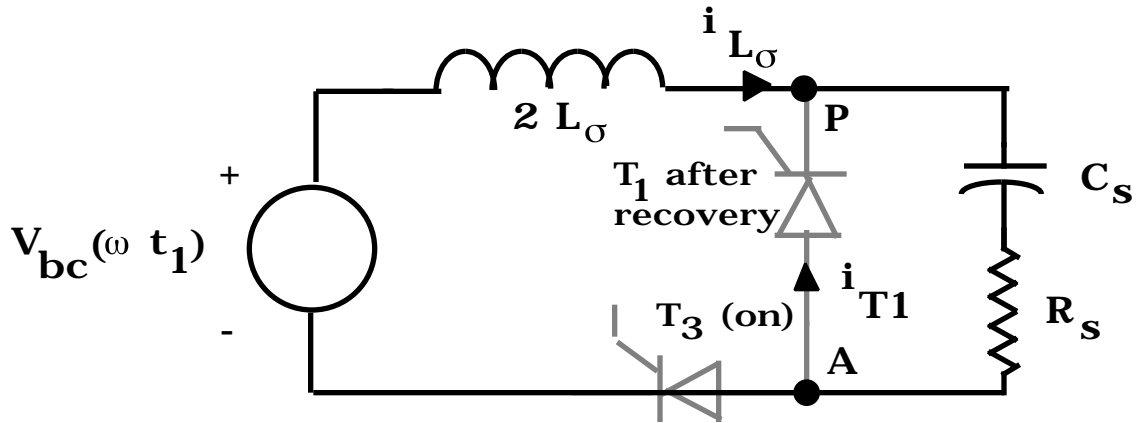- Equivalent circuit after T1 reverse recovery



- Assumptions

- Trigger angle $\alpha = 90^\circ$ so that $v_{LL}(t) = \text{maximum} = \sqrt{2} V_{LL}$
- Reverse recovery time $t_{rr} \ll \text{period of ac waveform}$ so that $v_{LL}(t)$ equals a constant value of $v_{bc}(t_1) = \sqrt{2} V_{LL}$
- Worst case stray inductance L gives rise to reactance equal to or less than 5% of line impedance.

- Line impedance $= \frac{V_s}{\sqrt{2}I_{a1}} = \frac{\sqrt{2}V_{LL}}{\sqrt{6}I_{a1}} = \frac{V_{LL}}{\sqrt{3}I_{a1}}$

where I_{a1} = rms value of fundamental component of the line current.

- $L = 0.05 \frac{V_{LL}}{\sqrt{3}I_{a1}}$

Component Values for Thyristor Snubber

- Use same design as for diode snubber but adapt the formulas to the thyristor circuit notation

- Snubber capacitor $C_S = C_{\text{base}} = L \frac{I_{rr}^2}{V_d}$

- From snubber equivalent circuit $2L \frac{di_L}{dt} = \sqrt{2} V_{LL}$

- $I_{rr} = \frac{di_L}{dt} t_{rr} = \frac{\sqrt{2} V_{LL}}{2L} t_{rr} = \frac{\sqrt{2} V_{LL}}{0.05 \frac{V_{LL}}{\sqrt{3} I_{a1}}} t_{rr} = 25 I_{a1} t_{rr}$

- $V_d = \sqrt{2} V_{LL}$

- $C_S = C_{\text{base}} = \frac{0.05 V_{LL}}{\sqrt{3} I_{a1}} \frac{25 I_{a1} t_{rr}}{\sqrt{2} V_{LL}}^2 = \frac{8.7 I_{a1} t_{rr}}{V_{LL}}$

- Snubber resistance $R_S = 1.3 R_{\text{base}} = 1.3 \frac{V_d}{I_{rr}}$

- $R_S = 1.3 \frac{\sqrt{2} V_{LL}}{25 I_{a1} t_{rr}} = \frac{0.07 V_{LL}}{I_{a1} t_{rr}}$

- Energy dissipated per cycle in snubber resistance = W_R

- $W_R = \frac{L I_{rr}^2}{2} + \frac{C_S V_d^2}{2} = 18 I_{a1} V_{LL} (t_{rr})^2$